

**EEE 3530  
Spring 2023**

**Project #3: Pipelined RISC-V Implementation**

**Objectives:**

To learn the basic structure and operation of the pipelined RISC-V processor

**Due Dates:**

Softcopy: June 14<sup>th</sup>, 23:59 PM (To LearnUS YONSEI)

*\* Late submission within 24 hours automatically deducts 20 percents of the point.*

**Things to Submit:**

1. Cover page with your name and Student ID
2. Schematic diagrams and codes printed from Quartus II (your design)
3. Simulation results and analysis (the waveform & answers to the questions)
4. Discussion

*\* In the report paper, working out must be shown.*


**Professor: W. W. Ro**

**T. A.: Seokjin Go, Dongin Lee, and  
Kyeonghoon Lim**

Feel free to contact us whenever you meet some difficulties or errors in the manual  
(but, spend some time and efforts to figure them out for yourself first)
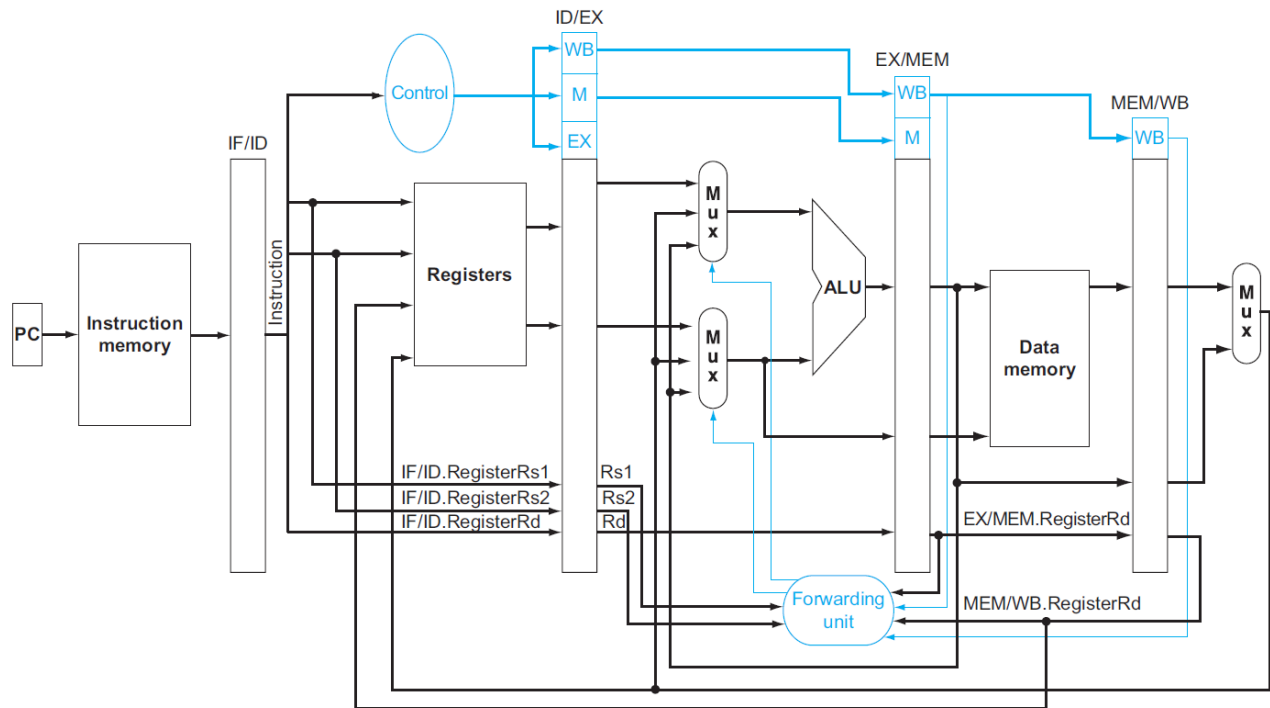
### 64-Bit Pipelined RISC-V Microprocessor Design

In project #2, we implemented the single-cycle RISC-V processor. Now, we will implement the pipelined RISC-V processor with forwarding operation. The processor architecture is shown in the figure below. This figure is identical to Fig. 4.54 in the textbook.




The requirement for the project is to implement and complete the datapath and control logic for pipelined architecture; major tasks include completion of the design and simulation of the 7 instructions: `add`, `sub`, `and`, `or`, `sd`, `ld`, and `beq`. The operation of each instruction follows the descriptions given in the textbook.


The design is implemented hierarchically with several block structures. Each block's operation and internal structure are identical to the descriptions in the textbook.

## File download and setup procedure

 
1. Copy the following 28 files (You can download the files from the class website) to your working directory for the project.



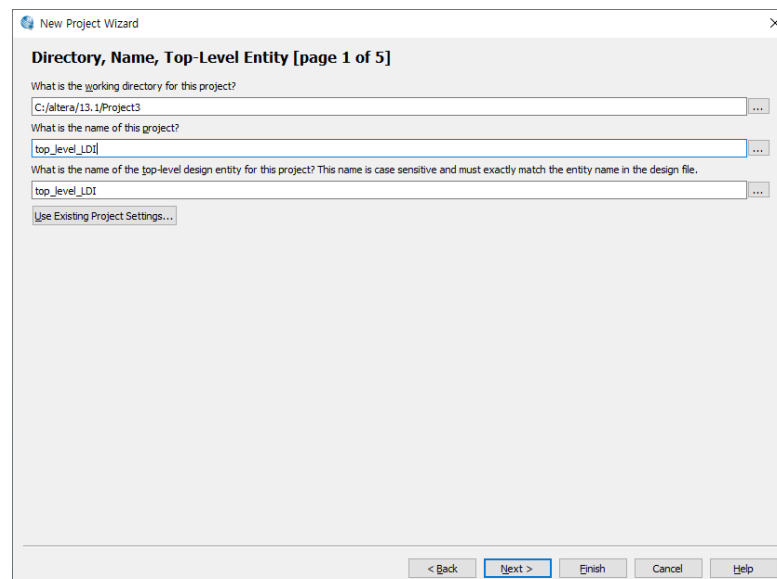
2. Change the file “project3\_WRO.bdf” to “top\_level\_your initial.bdf”.
3. Start Quartus II and go to “File” → “New Project Wizard”.
4. In the following window, find the working directory that you saved the 28 files in. Then, give the project name and the top-level design name as you named in step 2 (actually, **you can find the file and click that**).



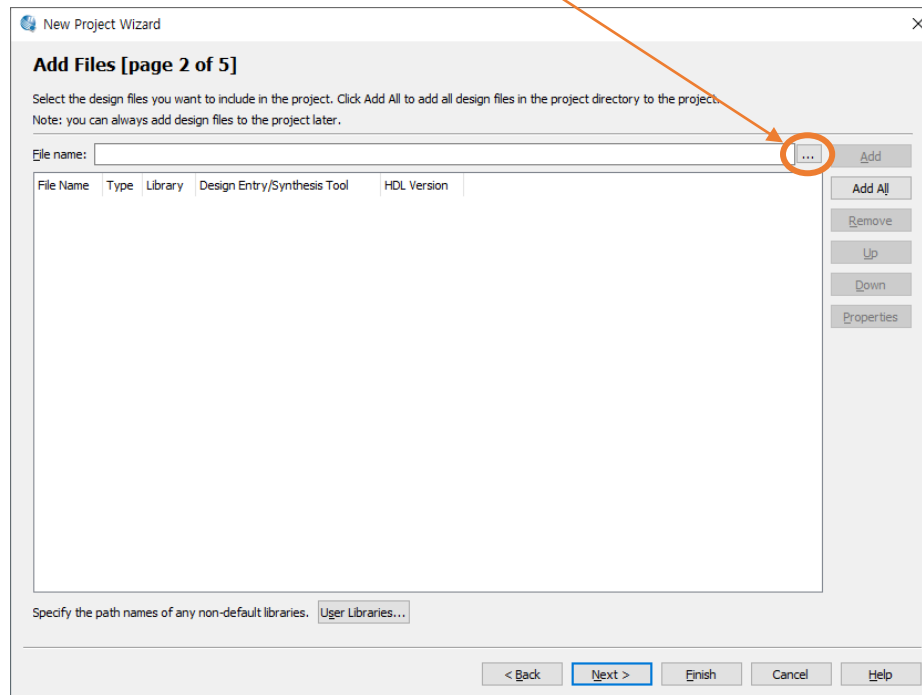
5. Then, in the following window, click here on this point. You need to locate your working directory.



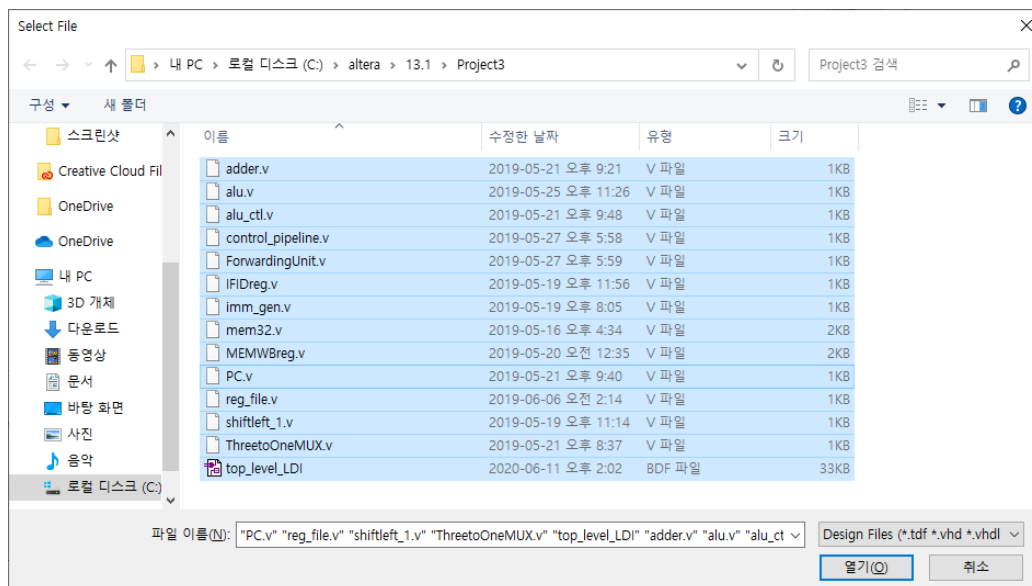
6. In the following window, select the 14 files.



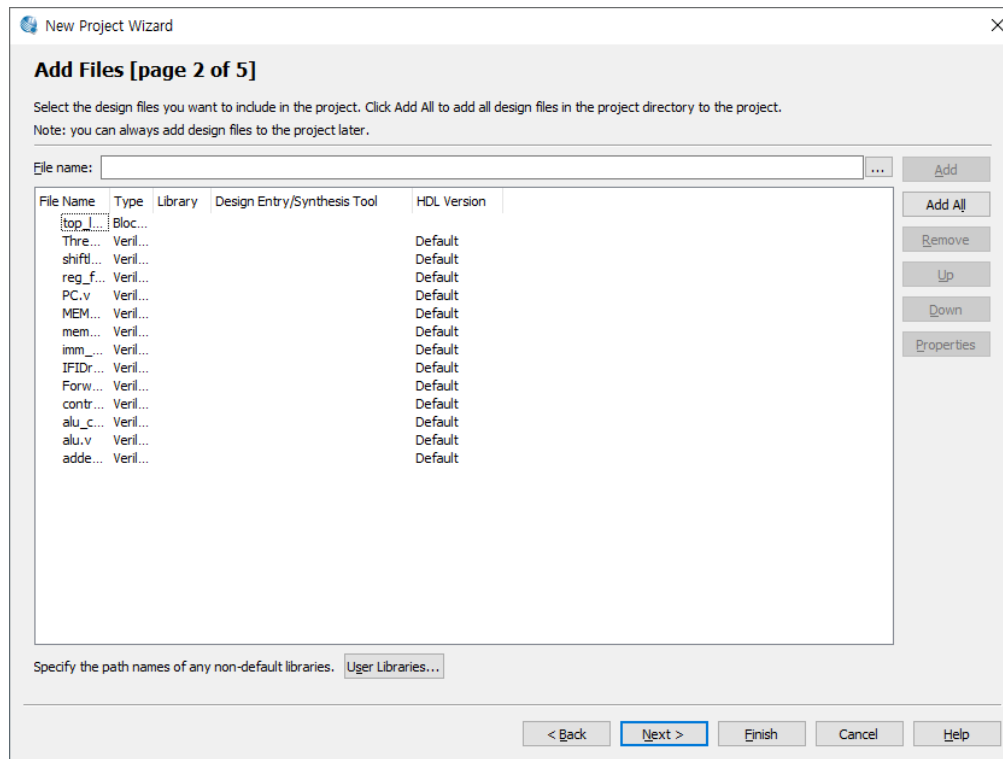7. Then, you will see the following box pop up. Just click “Next”.



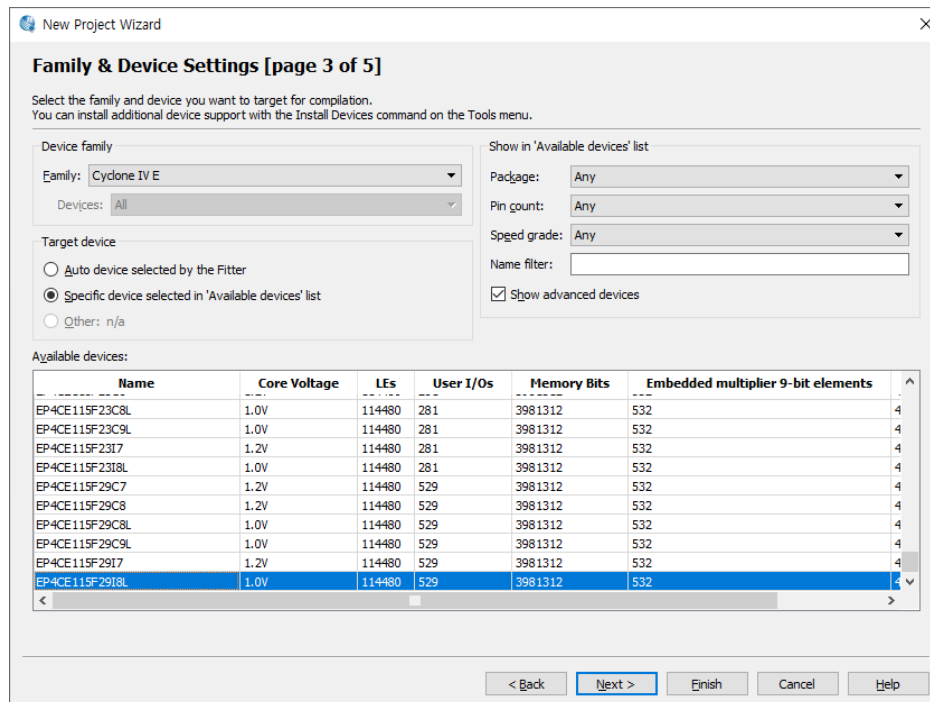
8. In the next pop-up window, choose ‘Device Family: Cyclone IV E, Device: EP4CE115F29I8L’.



9. Just select the “Next” buttons until you get to the following window.




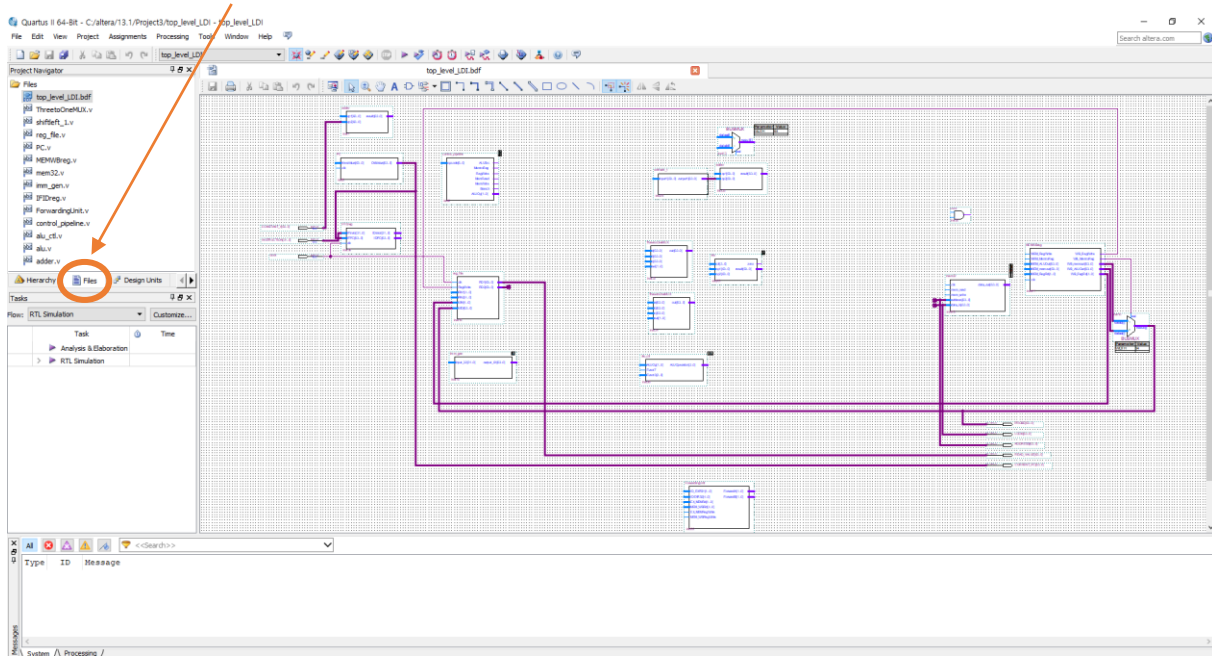10. Now, click the “Files” and double-click the “*top\_level\_your initial.bdf*” file.



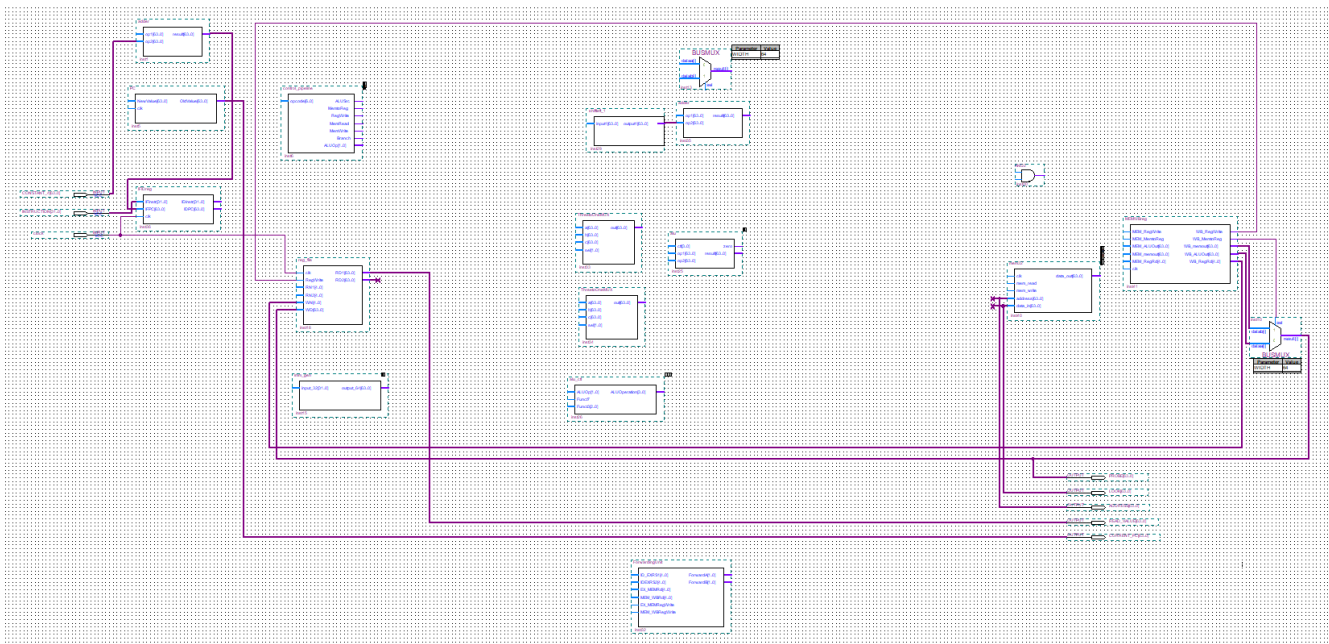11. Now the following diagram is an incomplete version of the pipelined RISC-V design.

(You should connect the disconnected parts)



\* The top-level file contains a special part (e.g., 5 output buses) for the simulation purpose, which is not included in the original design of the textbook.

- There are 5 output buses: "PROBE", "LOOK", "ADDRESS", "CURRENT\_PC" and "READ\_VALUE". Those five signals are inserted in the original design to probe each point of the circuit. Our simulation can show run-time signals for those five points.


12. Double-click the blocks and fill in the blanks in the source code. You can change the design of the existing modules for the correct operations.

(1) control\_pipeline.v

(2) ForwardingUnit.v

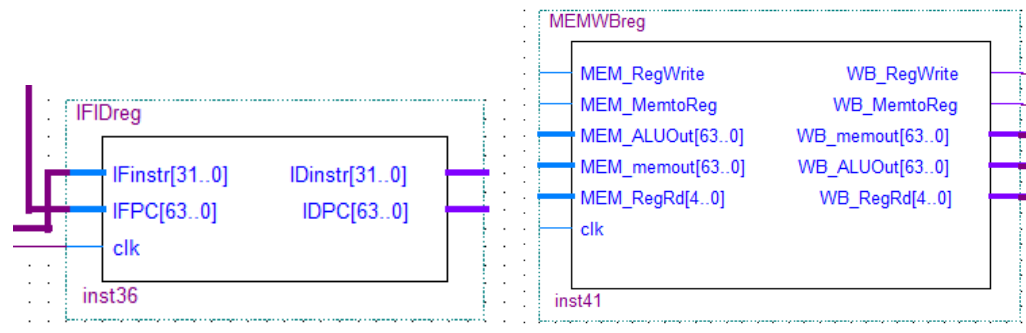13. You should make some pipeline registers to store the necessary values in ID/EX and EX/MEM.


The pipeline registers for IF/ID and MEM/WB are included in the source codes. You should make the new pipeline registers for the remaining stages based on the given registers.



You should determine the input and output ports of new registers by yourself. Moreover, the operation should be modified according to the changed input and output.

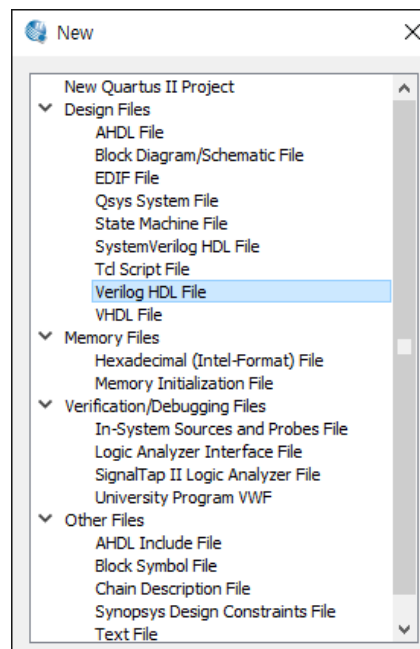14. You can include some other functional blocks to complete the design.

- If you verify that the given top module design doesn't have any blocks to implement pipelined RISC-V architecture, you may add some functional blocks to complete the design. You can see **“Create symbol files for this file”** by right-clicking on the file name in your project file list window after you complete and save the source code of a new module. When you save the source code, **be sure that the file name is the same as the module name.**





**Simulation:**

We provide a sequence of instructions to simulate. Also, we provide the list of initial values of the register file so that the given instruction sequence can be executed properly. The initial values are given in the table below. **Notice that you don't need to initialize the PC and the register file.**

**Initial Values**

Register No.	Initial Value	Register No.	Initial Value
x0	0	x4	8
x1	20	x5	30
x2	16	x6	2
x3	10	PC	0xA0000000

The instruction sequence is given in the table below. The instructions are given in the assembly codes, and you need to translate the instruction to the corresponding binary code for the simulation. These instructions are executed in the order shown below. You just show the correct output, not the real operation in RISC-V (**i.e., Do not jump to the target address in *beq* instructions, just show the output value**). You should refer to the last page of this document for **OPCODE** and **FUNCT** code.

**Instruction Sequence**

Sequence	Instruction
1	add x3, x1, x2
2	and x1, x2, x3
3	sub x5, x3, x1
4	sd x4, 12(x5)
5	or x5, x6, x4
6	and x1, x5, x4
7	beq x1, x3, 0x440
8	ld x6, 38(x5)
9	Your own example
10	Your own example

Also, you should answer the following two questions;

- (1) Compare the implementation without the forwarding unit and the one with the forwarding unit. Compare and explain the differences between the two results. You can explain the question by pointing out the wrong operations when the forwarding unit is not used.
- (2) Is the branch instruction (Instruction 7, beq) taken or not? If taken, how many instructions will be nop? Also, explain the appropriate method to resolve this problem(briefly). You can use any simulation results to support your answer. Note that you don't have to implement 'nop(flush)' operation.

Things to turn in:

- (1) Submit a soft copy of your report. The report should include the schematic design of your top module, source codes, a handful of discussions, and **simulation results (including the waveform).**
- (2) Also, upload a compressed file of all the files given (whether modified or not, all of them) and added to the class web page. Please match the format *Name(Korean)\_StudentID.zip*.
- (3) Analysis of the simulation results must be included to the report. You should completely describe and analyze the results and it should be written **in English.**

Format	Instruction	Opcode	Funct3	Funct6/7
R-type	add	0110011	000	0000000
	sub	0110011	000	0100000
	sll	0110011	001	0000000
	xor	0110011	100	0000000
	srl	0110011	101	0000000
	sra	0110011	101	0000000
	or	0110011	110	0000000
	and	0110011	111	0000000
	lr.d	0110011	011	0001000
I-type	sc.d	0110011	011	0001100
	lb	0000011	000	n.a.
	lh	0000011	001	n.a.
	lw	0000011	010	n.a.
	ld	0000011	011	n.a.
	lbu	0000011	100	n.a.
	lhu	0000011	101	n.a.
	lwu	0000011	110	n.a.
	addi	0010011	000	n.a.
	slli	0010011	001	0000000
	xori	0010011	100	n.a.
	srlr	0010011	101	0000000
	srai	0010011	101	0100000
	ori	0010011	110	n.a.
	andi	0010011	111	n.a.
S-type	jalr	1100111	000	n.a.
	sb	0100011	000	n.a.
	sh	0100011	001	n.a.
	sw	0100011	010	n.a.
SB-type	sd	0100011	111	n.a.
	beq	1100111	000	n.a.
	bne	1100111	001	n.a.
	blt	1100111	100	n.a.
	bge	1100111	101	n.a.
	bltu	1100111	110	n.a.
U-type	bgeu	1100111	111	n.a.
	lui	0110111	n.a.	n.a.
UJ-type	jal	1101111	n.a.	n.a.